

Problem 1. (Problem 2.1 on page 47 of the text.) In Figure 2.1,

$$v(t) = \sqrt{2} \cdot 120 \cdot \cos(\omega \cdot t + 30 \cdot \text{deg}) \quad i(t) = \sqrt{2} \cdot 10 \cdot \cos(\omega \cdot t - 30 \cdot \text{deg})$$

- Find $p(t)$, S , P , and Q into the network.
- Find a simple, two element, series circuit consistent with the prescribed terminal behavior as described in this problem.

$$p(t) = v(t) \cdot i(t)$$

$$p(t) = 2400 \cdot \cos(\omega \cdot t + 30 \cdot \text{deg}) \cdot \cos(\omega \cdot t - 30 \cdot \text{deg})$$

$$p(t) = 1200 \cdot (\cos(60 \cdot \text{deg}) + \cos(2 \cdot \omega \cdot t))$$

$$p(t) = 600 + 1200 \cdot \cos(2 \cdot \omega \cdot t)$$

$$j := \sqrt{-1}$$

Use RMS Phasors

$$V := 120 \cdot e^{j \cdot 30 \cdot \text{deg}} \cdot \text{volt} \quad I := 10 \cdot e^{-j \cdot 30 \cdot \text{deg}} \cdot \text{A}$$

Calculate the power quantities

$$\text{VAr} := \text{volt} \cdot \text{amp}$$

$$S := V \cdot \bar{I} \quad S = 600 + 1039i \text{ volt} \cdot \text{amp}$$

$$P := \text{Re}(S) \quad P = 600 \text{ W}$$

$$Q := \text{Im}(S) \quad Q = 1.039 \times 10^3 \text{ VAr}$$

To find the series circuit, first find the equivalent impedance. The series circuit will be two elements, a resistor to model the real part of the impedance and a reactance (in this case, an inductive reactance, to model the reactive portion.

$$Z := \frac{V}{I} \quad Z = 6 + 10.392i \text{ ohm}$$

6 ohms 10.39 ohms



Problem 2. (problem 2.4 on page 48). A 3phase load draws 200 kW at a PF of 0.707 lagging from a 440-V line. In parallel is a 3phase capacitor bank which supplies 50 kVAR. Find the resultant power factor and current into the parallel combination.

$$P_i := 200 \cdot \text{kW} \quad \text{PF}_i := 0.707 \quad V_{LLi} := 440 \cdot \text{volt} \quad Q_{\text{cap}} := 50 \cdot \text{kV} \cdot \text{A}$$

Find the initial values of apparent power S and reactive power Q

$$S_i := \frac{P_i}{\text{PF}_i} \quad Q_i := \sqrt{S_i \cdot S_i - P_i \cdot P_i} \quad Q_i = 200.06 \cdot \text{kV} \cdot \text{A}$$

Real power P is unchanged by addition or deletion of reactive power Q.

$$P_f := P_i \quad P_f = 2 \cdot 10^5 \text{ W}$$

Add the two reactive power components together. Capacitive reactive power is negative under the convention assumed in the text.

$$Q_f := Q_i + (-Q_{\text{cap}}) \quad Q_f = 150.06 \cdot \text{kV} \cdot \text{A}$$

Calculate the new apparent power. The power factor is the ratio of real power to apparent power.

$$S_f := \sqrt{P_f \cdot P_f + Q_f \cdot Q_f} \quad S_f = 250.036 \cdot \text{kV} \cdot \text{A}$$


$$\text{PF}_f := \frac{P_f}{S_f} \quad \text{PF}_f = 0.8 \quad \text{lagging}$$

Use a three phase power formula to find the line current.

$$I_a := \frac{S_f}{\sqrt{3} \cdot V_{LLi}} \quad I_a = 328 \text{ A}$$

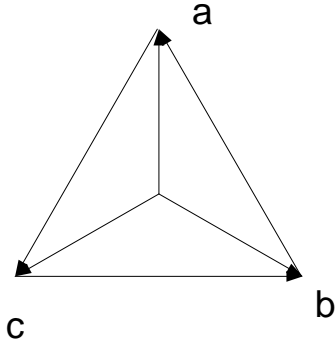Problem 3. (Problem 2.6 on page 47) The system shown in the Figur below is balanced and positive sequence. Assume that $Z=10$ at 15 deg and $V_{ca}=208$ at -120 deg. Find V_{ab} , V_{bc} , V_{an} , V_{bn} , V_{cn} , I_a , I_b , I_c , and $S_{3\text{phase}}$.

Use a phasor diagram with a horizontal zero reference and counterclockwise positive direction:



Phase angles, by inspection:

given $\theta_{ca} := -120\text{-deg}$

$\theta_{ab} := 120\text{-deg}$ $\theta_{an} := 90\text{-deg}$

$\theta_{bc} := 0\text{-deg}$ $\theta_{bn} := -30\text{-deg}$

$\theta_{cn} := -150\text{-deg}$

A balanced system has the given 208V between any pair of lines; So, between line and neutral,

$$V_{an} := \left[\frac{208}{\sqrt{3}} \cdot (\cos(\theta_{an}) + j \cdot \sin(\theta_{an})) \right] \text{ volt} \quad |V_{an}| = 120.1 \text{ volt} \quad j := \sqrt{-1}$$

The other two line-to-neutral voltages have the same magnitude. The phase angle of V_{an} , from the phasor diagram, is 90 degrees. The other two line-to-neutral voltages have phase angles as given beside the diagram above. Therefore, the balanced system has 120.1V line to neutral in each phase.

Current is voltage divided by impedance.

$$Z := 10 \cdot e^{-j \cdot 15\text{-deg}} \cdot \text{ohm} \quad I_a := \frac{V_{an}}{Z} \quad |I_a| = 12 \text{ A}$$

$$\phi_a := \text{angle}(\text{Re}(I_a), \text{Im}(I_a)) \quad \phi_a = 105\text{-deg}$$

Phase angles on the other two line currents are

$$\phi_b := \phi_a - 120\text{-deg} \quad \phi_b = -15\text{-deg} \quad \phi_c := \phi_a + 120\text{-deg} \quad \phi_c = 225\text{-deg}$$


Three phase complex power is

$$S_{3\phi} := 3 \cdot V_{an} \cdot \overline{I_a} \quad S_{3\phi} = 4179 - 1120i \text{ volt} \cdot \text{amp}$$

Summary of answers:

All line-to-neutral voltages are 120.1 Volts. All line-to-line voltages are 208 Volts. All line currents are 12.0 A.

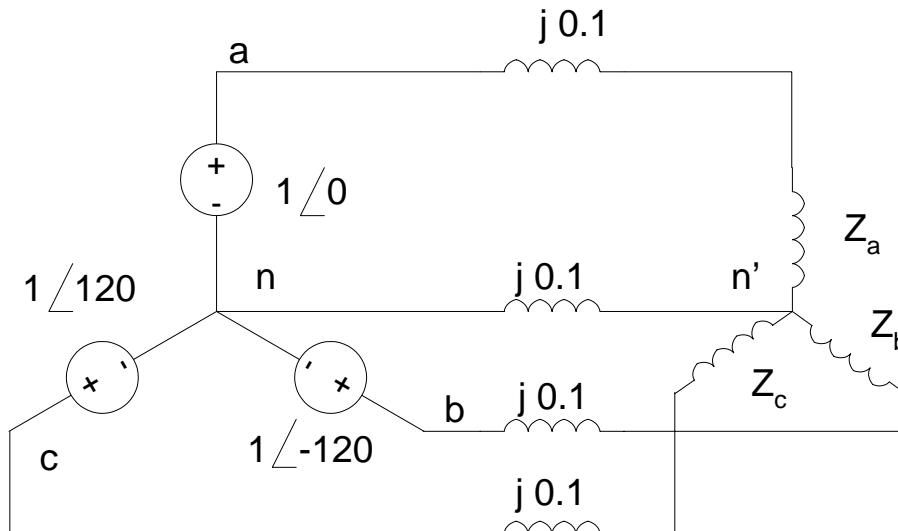- Problem 4. (Problem 2.8 on page 47) In the system shown in the figure below, find I_a , I_b , and I_c for
- $Z_a=j1$; $Z_b=j1$; $Z_c=j0.9$ (unbalanced)
 - $Z_a=j1$; $Z_b=j1$; $Z_c=j1$ (balanced)



Write down the given.

$$j := \sqrt{-1}$$

$$V_{an} := 1.0 \quad V_{bn} := 1.0 \cdot e^{-j \frac{2\pi}{3}} \quad V_{cn} := 1.0 \cdot e^{j \frac{2\pi}{3}}$$

$$Z_{line} := j \cdot 0.1 \quad Z_a := j \cdot 1 \quad Z_b := j \cdot 1 \quad Z_c := j \cdot 0.9$$

The mesh equations are as follows:

$$V_{an} = I_a \cdot Z_{line} + I_a \cdot Z_a + (I_a + I_b + I_c) \cdot Z_{line}$$

$$V_{bn} = I_b \cdot Z_{line} + I_b \cdot Z_b + (I_a + I_b + I_c) \cdot Z_{line}$$

$$V_{cn} = I_c \cdot Z_{line} + I_c \cdot Z_c + (I_a + I_b + I_c) \cdot Z_{line}$$

Forming into a matrix

$$\begin{bmatrix} Z_{line} + Z_a + Z_{line} & Z_{line} & Z_{line} \\ Z_{line} & Z_{line} + Z_b + Z_{line} & Z_{line} \\ Z_{line} & Z_{line} & Z_c + Z_{line} + Z_{line} \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix}$$

Inverting the matrix to solve,

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} := \begin{bmatrix} Z_{\text{line}} + Z_a + Z_{\text{line}} & Z_{\text{line}} & Z_{\text{line}} \\ Z_{\text{line}} & Z_{\text{line}} + Z_b + Z_{\text{line}} & Z_{\text{line}} \\ Z_{\text{line}} & Z_{\text{line}} & Z_c + Z_{\text{line}} + Z_{\text{line}} \end{bmatrix}^{-1} \begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix}$$

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} -5.584 \cdot 10^{-3} - 0.912i \\ -0.793 + 0.451i \\ 0.86 + 0.496i \end{bmatrix}$$

$$|I_a| = 0.912 \quad \text{angle}(\text{Re}(I_a), \text{Im}(I_a)) - 360 \cdot \text{deg} = -90.351 \text{ deg}$$

$$|I_b| = 0.912 \quad \text{angle}(\text{Re}(I_b), \text{Im}(I_b)) - 360 \cdot \text{deg} = -209.649 \text{ deg}$$

$$|I_c| = 0.993 \quad \text{angle}(\text{Re}(I_c), \text{Im}(I_c)) = 30 \text{ deg}$$

Same process for the balanced system,

$$Z_{\text{line}} := j \cdot 0.1 \quad Z_a := j \cdot 1 \quad Z_b := j \cdot 1 \quad Z_c := j \cdot 1.0$$

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} := \begin{bmatrix} Z_{\text{line}} + Z_a + Z_{\text{line}} & Z_{\text{line}} & Z_{\text{line}} \\ Z_{\text{line}} & Z_{\text{line}} + Z_b + Z_{\text{line}} & Z_{\text{line}} \\ Z_{\text{line}} & Z_{\text{line}} & Z_c + Z_{\text{line}} + Z_{\text{line}} \end{bmatrix}^{-1} \begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix}$$

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} -0.909i \\ -0.787 + 0.455i \\ 0.787 + 0.455i \end{bmatrix}$$

$$|I_a| = 0.909 \quad \text{angle}(\text{Re}(I_a), \text{Im}(I_a)) - 360 \cdot \text{deg} = -90 \text{ deg}$$

$$|I_b| = 0.909 \quad \text{angle}(\text{Re}(I_b), \text{Im}(I_b)) - 360 \cdot \text{deg} = -210 \text{ deg}$$

$$|I_c| = 0.909 \quad \text{angle}(\text{Re}(I_c), \text{Im}(I_c)) = 30 \text{ deg}$$

It is also possible (and easier) to solve the balanced system using a per phase equivalent.

$$I_a := \frac{V_{an}}{Z_{line} + Z_a} \quad I_a = -0.909i \quad |I_a| = 0.909 \quad \text{angle}(\text{Re}(I_a), \text{Im}(I_a)) = 270^\circ \text{deg}$$


$$I_b := \frac{V_{bn}}{Z_{line} + Z_b} \quad I_b = -0.787 + 0.455i \quad |I_b| = 0.909 \quad \text{angle}(\text{Re}(I_b), \text{Im}(I_b)) = 150^\circ \text{deg}$$

$$I_c := \frac{V_{cn}}{Z_{line} + Z_c} \quad I_c = 0.787 + 0.455i \quad |I_c| = 0.909 \quad \text{angle}(\text{Re}(I_c), \text{Im}(I_c)) = 30^\circ \text{deg}$$

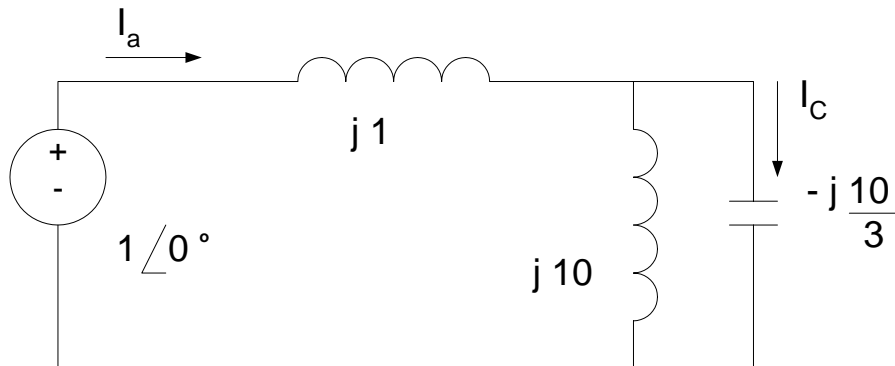Problem 5. (Problem 2.12 on page 49 of the text) The system shown below is balanced. Assume that load inductors $Z_L=j10$ and load capacitors $Z_C=-j10$. Find I_a , I_{cap} , and $S_{3\phi load}$.

$$Z_{C\Delta} := -j \cdot 10 \quad Z_{LY} := j \cdot 10 \quad j := \sqrt{-1}$$

It is probably easiest to convert to a Y equivalent circuit. The per phase equivalent circuit becomes:



The delta to wye conversion reduces the balanced capacitance by a factor of 3. Finding the current I_a :

$$Z_{load} := \frac{(j \cdot 10) \cdot \left(-j \cdot \frac{10}{3}\right)}{j \cdot 10 - j \cdot \frac{10}{3}} \quad Z_{load} = -5i \quad I_a := \frac{1.0 + j \cdot 0.0}{j \cdot 1 + Z_{load}} \quad I_a = 0.25i$$

By current division,

$$I_C := I_a \cdot \frac{(j \cdot 10)}{j \cdot 10 - j \cdot \frac{10}{3}} \quad I_C = 0.375i$$

the current in a delta is a factor of $\sqrt{3}$ less than the equivalent wye current and leads by 30 degrees.

$$I_{cap} := \frac{I_C}{\sqrt{3}} e^{j \frac{\pi}{6}} \quad I_{cap} = -0.108 + 0.188i \quad |I_{cap}| = 0.217$$

$$I_{cap_angle} := \text{angle}(\text{Re}(I_{cap}), \text{Im}(I_{cap})) \quad I_{cap_angle} = 120^\circ \text{deg}$$

Finding the three phase output complex power (in this case all reactive),

$$S_{3\phi load} := 3 \cdot |I_a| \cdot |I_a| \cdot Z_{load} \quad S_{3\phi load} = -0.9375i$$

Checking the complex power out,


$$V_{\text{anx}} := I_a \cdot Z_{\text{load}}$$

$$S_{3\phi\text{load}} := 3 \cdot V_{\text{anx}} \cdot \overline{I_a} \quad S_{3\phi\text{load}} = -0.937i$$

Another check of complex power out,

$$S_{3\phi\text{in}} := 3 \cdot 1 \cdot \overline{I_a} \quad S_{3\phi\text{out}} := S_{3\phi\text{in}} - 3 \cdot |I_a| \cdot |I_a| \cdot (j \cdot 1) \quad S_{3\phi\text{out}} = -0.937i$$

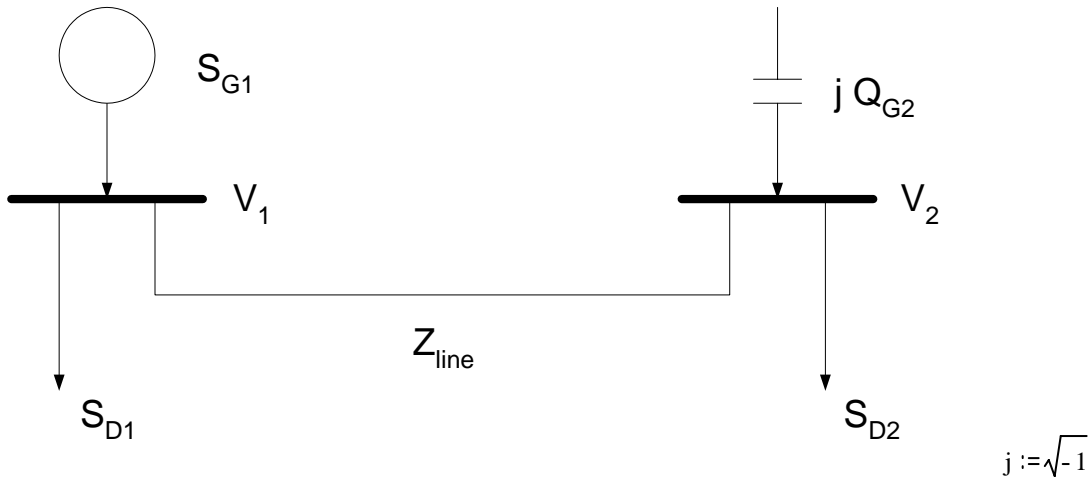Problem 6. In the Figure shown below, assume that



$$V_1 := 1 + j \cdot 0$$

$$Z_{\text{line}} := 0.01 + j \cdot 0.1$$

$$S_{D1} := 0.5 + j \cdot 0.5$$

$$S_{D2} := 0.5 + j \cdot 0.5$$

$$j := \sqrt{-1}$$

Pick QG2 such that $|V_2|=1$. In this case, what are QG2, SG1, and the angle of V2?

State the given voltage magnitude and find the angle on the line impedance.

$$V_{2\text{mag}} := 1 \quad \text{angle}_Z := \text{angle}(\text{Re}(Z_{\text{line}}), \text{Im}(Z_{\text{line}})) \quad \text{angle}_Z = 84.289^\circ \text{deg}$$

From the diagram, we see that the real power in the load SD2 must all be supplied from the transmission line.

$$P_{D2} := \text{Re}(S_{D2}) \quad P_{D2} = 0.5$$

$$P_{21} := -P_{D2} \quad P_{21} = -0.5$$

An expression for the real power from the line is as follows:

$$P_{21} = \text{Re} \left[\frac{(|V_2|)^2}{|Z_{\text{line}}|} \cdot e^{j \cdot \text{angle}_Z} - \frac{|V_1| \cdot V_{2\text{mag}}}{|Z_{\text{line}}|} \cdot e^{j \cdot \text{angle}_Z} \cdot e^{j \cdot \theta_{12}} \right]$$

Guess

$$\theta_{12} := 0^\circ \text{deg}$$

Take the real part and solve for the voltage phase angle difference across the transmission line.

Given

$$P_{21} = \frac{(|V_{2\text{mag}}|)^2}{|Z_{\text{line}}|} \cdot \cos(\text{angle}_Z) - \frac{|V_1| \cdot V_{2\text{mag}}}{|Z_{\text{line}}|} \cdot \cos(\text{angle}_Z + \theta_{12})$$

$$\theta_{12} := \text{Find}(\theta_{12}) \quad \theta_{12} = -2.902^\circ \text{deg}$$

Therefore, **voltage V2 is 1.0 at an angle of - 2.902 degrees.**

A rectangular form to be used in calculations that follow is

$$V_2 := V_{2\text{mag}} \cdot (\cos(\theta_{12}) + j \cdot \sin(\theta_{12}))$$

An expression derived in class for S12 is

$$S_{12} := \frac{(|V_1|)^2}{Z_{\text{line}}} - \frac{|V_1| |V_2|}{Z_{\text{line}}} \cdot \overline{(e^{j \cdot \theta_{12}})}$$

solving,

$$S_{12} = 0.503 - 0.037i$$

At bus 1, the complex power balance is

$$S_{G1} := S_{D1} + S_{12} \quad S_{G1} = 1.003 + 0.463i$$

Therefore, **SG1 is 1.003 per unit real power and 0.463 per unit reactive power.**

At bus 2, the complex power entering is

$$S_{21} := \left[\frac{(|V_2|)^2}{Z_{\text{line}}} - \frac{|V_1| |V_2|}{Z_{\text{line}}} \cdot e^{j \cdot \theta_{12}} \right] \quad S_{21} = -0.5 + 0.063i$$

At bus 2, the complex power balance is

$$Q_{G2} := S_{21} + S_{D2} \quad Q_{G2} = -1.717 \cdot 10^{-7} + 0.563i$$

Therefore, **QG2 is 0.563 per unit reactive power.**