

Ex.4 Convolution (Response of electric circuits)

$R=3\Omega, L=1\text{ H}, C=0.5\text{ F}$


$R:=3 \quad L:=1 \quad C:=0.5 \quad Z(s):=R+s\cdot L+\frac{1}{s\cdot C}$

$\frac{1}{Z(s)} \xrightarrow{\text{invlaplace}} 2\cdot e^{-2\cdot t} - e^{-t} \quad h(t):=2\cdot e^{-2\cdot t} - e^{-t}$  impulse response

$e(t):=\Phi(t) \xrightarrow{\text{laplace}} \frac{1}{s} \quad E(s):=\frac{1}{s} \quad e(t):=\Phi(t)$  input

$I(s):=\frac{E(s)}{Z(s)} \rightarrow \frac{1}{s\cdot\left(s+\frac{2.0}{s}+3\right)} \xrightarrow{\text{invlaplace}} e^{-t} - e^{-(2\cdot t)}$  output

$i(t):=e^{-t} - e^{-(2\cdot t)}$  output

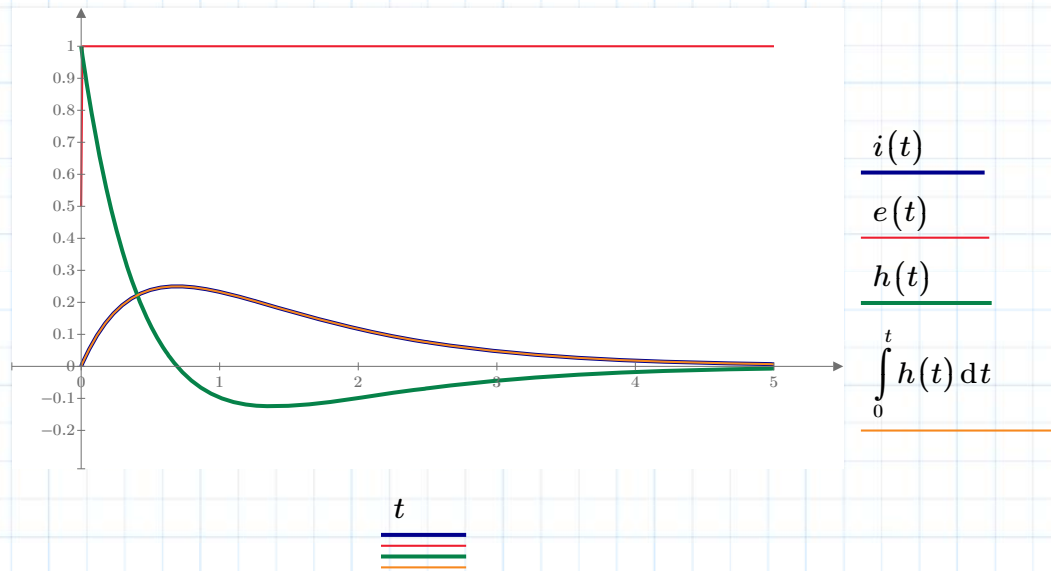

$h(t):=2\cdot e^{-2\cdot t} - e^{-t}$  impulse response

$h_i(t):=\int_0^t h(t) dt \rightarrow e^{-t} - e^{-(2\cdot t)}$  indicial response (unit step response)

```


推定値
R:=3 L:=1 C:=0.5
制約条件
1/C * q(t) + R * d/dt q(t) + L * d^2/dt^2 q(t) = Phi(t)    q(0)=0    q'(0)=0
ソルバ
q:=odesolve(q(t),5)
    
```



RLC Circuit (series connection)

$$Y(s) := \frac{1}{s + \frac{2.0}{s} + 3}$$
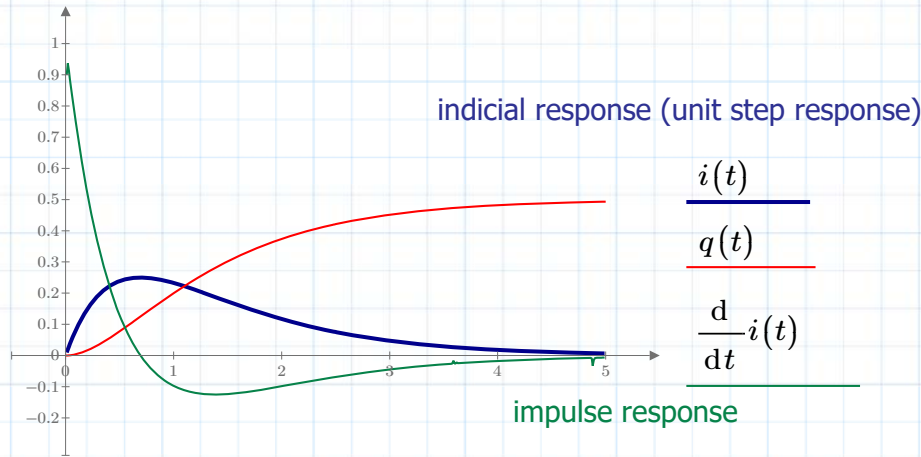
$$i(t) := \frac{d}{dt} q(t) \quad t := 0, 0.01 \dots 5$$



$t$

**clear(t)**

*input*

*output*

impulse response

$$\frac{d}{dt} \Phi(t) \xrightarrow{\text{laplace}} 1 \quad 2 \cdot e^{-2 \cdot t} - e^{-t} \quad \frac{1}{s + \frac{2.0}{s} + 3} \xrightarrow{\text{invlaplace}} 2 \cdot e^{-2 \cdot t} - e^{-t}$$

indicial response  
(unit step response)

$$\Phi(t) \xrightarrow{\text{laplace}} \frac{1}{s} \quad e^{-t} - e^{-(2 \cdot t)} \quad \frac{1}{s + \frac{2.0}{s} + 3} \xrightarrow{\text{invlaplace}} e^{-t} - e^{-(2 \cdot t)}$$

ramp response

$$\int_0^t \Phi(t) dt \xrightarrow{\text{laplace}} \frac{1}{s^2} \quad \frac{(e^{-t} - 1)^2}{2} \quad \frac{1}{s + \frac{2.0}{s} + 3} \xrightarrow{\text{invlaplace}} \frac{(e^{-t} - 1)^2}{2}$$

exponential response

$$e^{-2 \cdot t} \xrightarrow{\text{laplace}} \frac{1}{s + 2} \quad e^{-2 \cdot t} - e^{-t} + 2 \cdot t \cdot e^{-2 \cdot t} \quad \frac{1}{s + \frac{2.0}{s} + 3} \xrightarrow{\text{invlaplace}} e^{-2 \cdot t} - e^{-t} + 2 \cdot t \cdot e^{-2 \cdot t}$$