


Ex.S1 Response of electric circuit when impulse response and input signal are shown as follows. Sinusoidal waves input.  $R=1\Omega, L=1\text{ H}$  (Series connection)

$R:=1$        $L:=1$        $Z(s):=R+s\cdot L$        $h(t):=e^{-t}$       impulse response

$h(t):=e^{-t} \xrightarrow{\text{laplace}} \frac{1}{s+1}$        $H(s):=\frac{1}{s+1}$        $R:=1$        $\omega:=1$        $L:=1$

$H(\omega):=\int_0^{\infty} e^{-1\cdot\tau} \cdot e^{-1\cdot\omega\cdot\tau\cdot 1i} d\tau \xrightarrow{\text{simplify}} \frac{1}{1+\omega\cdot 1i}$

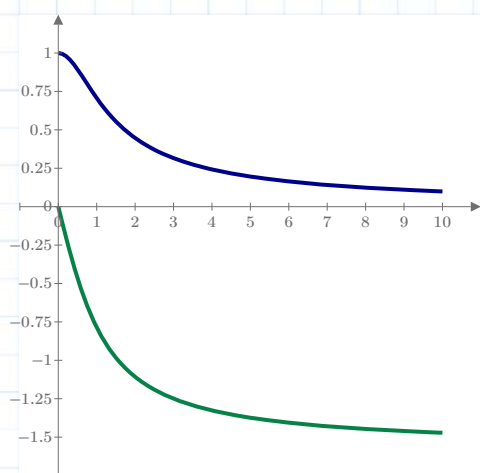$H(\omega):=\frac{1}{1+\omega\cdot 1i}$        $\omega:=0,0.1..10$



$H(1)=0.5-0.5i$

$|H(1)|=0.707$

$\arg(H(1))=-0.785$


$|H(\omega)|$

$\arg(H(\omega))$

$\omega$

$x(t):=\sin(t) + \sin(2\cdot t) + \sin(3\cdot t)$       input\_signal

$y(t):=|H(1)|\cdot\sin(t+\arg(H(1))) + |H(2)|\cdot\sin(2\cdot t+\arg(H(2))) + |H(3)|\cdot\sin(3\cdot t+\arg(H(3)))$   
output\_signal

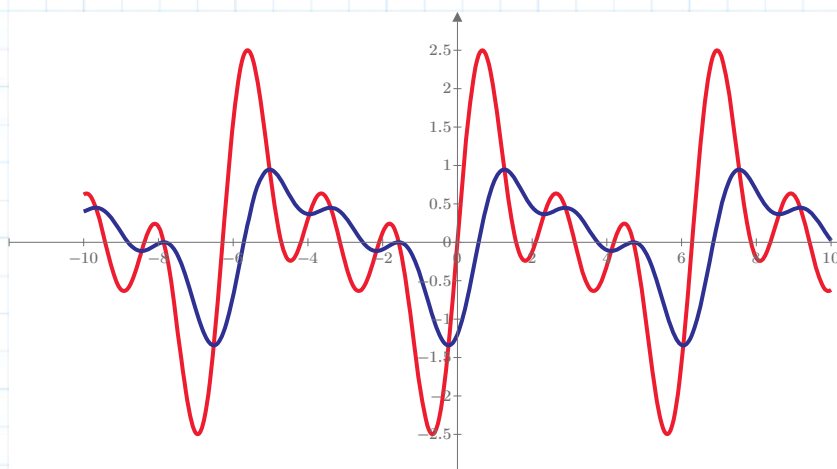

$x(t)$

$y(t)$

$t$