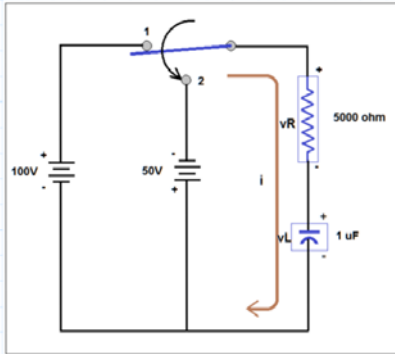


Solved Problem 7.23 (Energy function):

Obtain the energy function for the circuit of problem 7.22.



We found  $v_R$ :

$$v_R(t) := -150 \cdot e^{-200 \cdot t} \text{ V.}$$

We found  $v_C$ :

$$v_C(t) := 150 \cdot e^{-200 \cdot t} - 50 \text{ V.}$$

$$C := 1 \cdot 10^{-6} \text{ F}$$

$$R := 5000 \text{ Ohms}$$

$$R := 5000$$

$$C := 1 \cdot 10^{-6}$$

$$V_{C0} := 100 \quad V_{C\infty} := -50$$

$$v(t) := 50$$

$$I(s) := \frac{\frac{100}{s} + \frac{50}{s}}{R + \frac{1}{s \cdot C}}$$

$$i(t) := -I(s) \xrightarrow{\text{invlaplace}} \frac{-(3 \cdot e^{-(200 \cdot t)})}{100}$$

$$W_{C0} := \frac{1}{2} \cdot C \cdot V_{C0}^2 \rightarrow \frac{1}{200}$$

$$W_{C\infty} := \frac{1}{2} \cdot C \cdot V_{C\infty}^2 \rightarrow \frac{1}{800}$$


$$p(t) := i(t)^2 \cdot R \rightarrow \frac{9 \cdot (e^{-(200 \cdot t)})^2}{2} \quad W_R := \int_0^{\infty} p(t) dt \rightarrow \frac{9}{800}$$

$$q(t) := \int_0^t i(t) dt + C \cdot V_{C0} \rightarrow \frac{3 \cdot e^{-(200 \cdot t)} - 1}{20000}$$

$$v_C(t) := \frac{q(t)}{C}$$

$$v_R(t) := i(t) \cdot R$$

$$v(t) := v_C(t) + v_R(t)$$

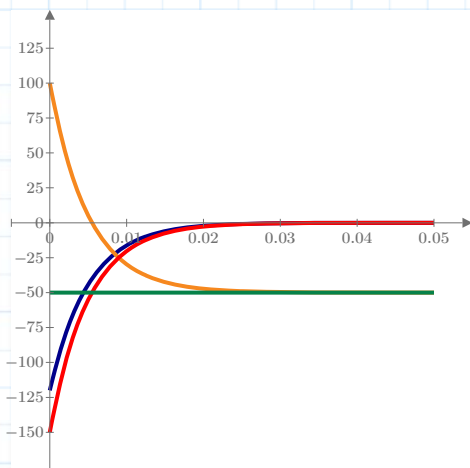

$$\begin{aligned} & i(t) \cdot 4000 \\ & v_C(t) \\ & v_R(t) \\ & v(t) \end{aligned} \quad \text{KV2}$$


t

$$p_{50}(t) := -50 \cdot i(t) \quad W_{50}(t) := \int_0^t p_{50}(\tau) d\tau \quad W_R(t) := \int_0^t p(\tau) d\tau$$

$$W_C(t) := \frac{1}{2} \cdot C \cdot v_C(t)^2 \rightarrow \frac{(150 \cdot e^{-(200 \cdot t)} - 50)^2}{2000000} \quad \frac{2500}{2000000} = 0.00125$$

$$W_R(t) := \int_0^t p(\tau) d\tau \rightarrow \frac{-(9 \cdot e^{-(400 \cdot t)}) + 9}{800} \quad \frac{9}{800} = 0.011$$

$$W(t) := -W_{50}(t) + W_R(t) + W_C(t)$$

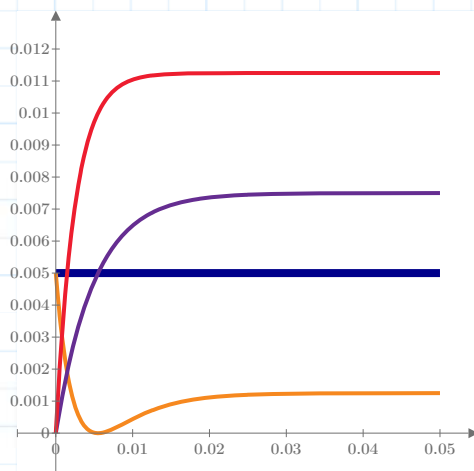

$t$



$$\frac{9}{800} \quad \frac{9-3}{800} \rightarrow \frac{3}{400}$$

$$W(t) \quad W_{50}(\infty) \rightarrow \frac{3}{400}$$

$$W_C(t) \quad \frac{1}{200} = 0.005 \quad \frac{1}{800} = 0.00125$$

$$W_{50}(t)$$

$$W_R(t)$$