

## Zeros and Poles of 2-nodes circuits

$$Z(s) := s \quad \text{Zeros}=0 \quad L_1 := 1$$

$$Z(s) := \frac{1}{s} \quad \text{Poles}=0 \quad C_1 := 1$$

$$Z(s) := \frac{(s^2 + 1)}{s} \xrightarrow{\text{parfrac}} s + \frac{1}{s} \quad L_1 := 1 \quad C_2 := 1 \quad \leftarrow \text{Series}$$

$$Z(s) := \frac{s}{(s^2 + 1)} \quad \text{Parallel}$$

$$\frac{1}{s + \frac{1}{s}} \xrightarrow{\text{factor}} \frac{s}{s^2 + 1} \quad C_1 := 1$$

$$L_1 := 1$$

$$Z(s) := \frac{(s^2 + 1)}{s \cdot (s^2 + 2)} \xrightarrow{\text{parfrac}} \frac{s}{2 \cdot (s^2 + 2)} + \frac{1}{2 \cdot s} \quad C_1 := 2 \quad L_2 := \frac{1}{2} \quad \leftarrow \text{Series}$$

$$\frac{1}{2 \cdot s + \frac{2}{s}} \xrightarrow{\text{factor}} \frac{s}{2 \cdot (s^2 + 1)} \quad C_2 := 2$$

Parallel

$$\text{Zeros } \omega = 0, \omega = \sqrt{2} \quad \text{Parallel}$$

$$Z(s) := \frac{s \cdot (s^2 + 2)}{(s^2 + 1)} \xrightarrow{\text{parfrac}} s + \frac{s}{s^2 + 1} \quad L_1 := 1 \quad C_2 := 1 \quad \leftarrow \text{Series}$$

$$\text{Poles } \omega = \sqrt{1} \quad L_2 := 1$$

$$\text{Zeros } \omega = \sqrt{1}, \omega = \sqrt{3}$$

$$Z(s) := \frac{(s^2 + 1) \cdot (s^2 + 3)}{s \cdot (s^2 + 2)} \xrightarrow{\text{parfrac}} s + \frac{s}{2 \cdot (s^2 + 2)} + \frac{3}{2 \cdot s}$$

$$\text{Poles } \omega = 0, \omega = \sqrt{2}$$

Parallel

$$L_1 := 1 \quad L_2 := \frac{1}{2} \quad C_3 := \frac{2}{3} \quad \leftarrow \text{Series}$$

$$C_2 := 2$$

Zeros  $\omega = 0, \omega = \sqrt{2}$

$$Z(s) := \frac{s \cdot (s^2 + 2)}{(s^2 + 1) \cdot (s^2 + 3)} \xrightarrow{\text{parfrac}} \frac{s}{2 \cdot (s^2 + 1)} + \frac{s}{2 \cdot (s^2 + 3)}$$

Poles  $\omega = \sqrt{1}, \omega = \sqrt{3}$

Parallel	Parallel	
$L_1 := \frac{1}{2}$	$C_2 := 1$	← Series
$C_1 := 2$	$L_2 := \frac{1}{6}$	

Zeros  $\omega = \sqrt{1}, \omega = \sqrt{3}$

$$Z(s) := \frac{(s^2 + 1) \cdot (s^2 + 3)}{s \cdot (s^2 + 2) \cdot (s^2 + 4)} \xrightarrow{\text{parfrac}} \frac{s}{4 \cdot (s^2 + 2)} + \frac{3 \cdot s}{8 \cdot (s^2 + 4)} + \frac{3}{8 \cdot s}$$

Poles  $\omega = 0, \omega = \sqrt{2}, \omega = \sqrt{4}$

Parallel	Parallel	
$L_1 := \frac{1}{8}$	$L_2 := \frac{3}{32}$	$C_3 := \frac{8}{3}$ ← Series
$C_1 := 4$	$C_2 := \frac{8}{3}$	

Zeros  $\omega = 0, \omega = \sqrt{2}, \omega = \sqrt{4}$

$$Z(s) := \frac{s \cdot (s^2 + 2) \cdot (s^2 + 4)}{(s^2 + 1) \cdot (s^2 + 3)} \xrightarrow{\text{parfrac}} s + \frac{3 \cdot s}{2 \cdot (s^2 + 1)} + \frac{s}{2 \cdot (s^2 + 3)}$$

Poles  $\omega = \sqrt{1}, \omega = \sqrt{3}$


Parallel	Parallel	
$L_1 := 1$	$C_2 := \frac{2}{3}$	$C_3 := 2$ ← Series
	$L_2 := \frac{3}{2}$	$L_3 := \frac{1}{6}$

9. LC 4 elements circuits

F1

$$Z(s) := \frac{(s^2 + 1)}{s} \cdot \frac{(s^2 + 9)}{(s^2 + 4)} \xrightarrow{\text{parfrac}} s + \frac{15 \cdot s}{4 \cdot (s^2 + 4)} + \frac{9}{4 \cdot s}$$
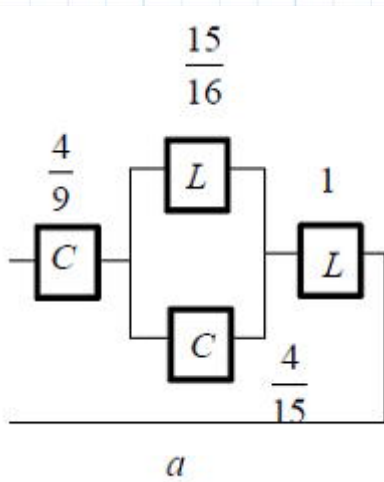
$$Z(s) := s + \frac{\frac{15}{4} \cdot s}{s^2 + 4} + \frac{9}{4 \cdot s} \quad C_0 := \frac{4}{9} \quad C := \frac{4}{15} \quad L := \frac{15}{16} \quad L_{\infty} := 1$$




```
clear(s, C, L)
s * L * 1 / (s * C) >> simplify >> L * s / (C * L * s^2 + 1)
s * L + 1 / (s * C)
L * s / (C * L * s^2 + 1) = s * 1 / (s^2 + 1 / (L * C))
```

F2

$$Y(s) := \frac{s}{(s^2 + 1)} \cdot \frac{(s^2 + 4)}{(s^2 + 9)} \xrightarrow{\text{parfrac}} \frac{3 \cdot s}{8 \cdot (s^2 + 1)} + \frac{5 \cdot s}{8 \cdot (s^2 + 9)}$$
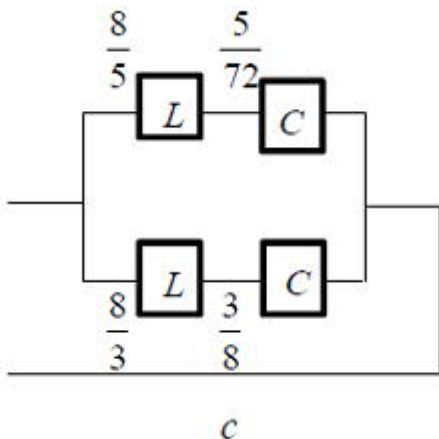
$$Y(s) := \frac{\frac{3}{8} \cdot s}{s^2 + 1} + \frac{\frac{5}{8} \cdot s}{s^2 + 9} \quad L_1 := \frac{8}{3} \quad C_1 := \frac{3}{8} \quad L_2 := \frac{8}{5} \quad C_2 := \frac{5}{72}$$




```
clear(s, C, L)
s * C * 1 / (s * L) >> simplify >> C * s / (C * L * s^2 + 1)
s * C + 1 / (s * L)
C * s / (C * L * s^2 + 1) = s * 1 / (s^2 + 1 / (L * C))
```

C1

$$Z(s) := \frac{(s^2 + 1)}{s} \cdot \frac{(s^2 + 9)}{(s^2 + 4)} \xrightarrow{\text{parfrac}} s + \frac{15 \cdot s}{4 \cdot (s^2 + 4)} + \frac{9}{4 \cdot s}$$

$$s + \frac{15 \cdot s}{4 \cdot (s^2 + 4)} \xrightarrow{\text{confrac, fraction}} \frac{s}{\frac{16}{31} + \frac{s^2}{\frac{961}{60} + \frac{s^2}{15}}}$$

$$C_1 := \frac{4}{9}$$

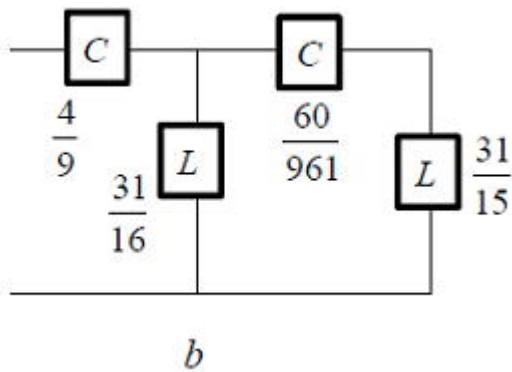

$$\frac{1}{s \cdot C_1} + \frac{1}{\frac{1}{s \cdot L_1} + \frac{1}{\frac{1}{s \cdot C_2} + s \cdot L_2}}$$

$$L_1 := \frac{31}{16}$$

$$C_2 := \frac{60}{961} \quad L_2 := \frac{31}{15}$$

$$\frac{s}{(s^2 + 1)} \cdot \frac{(s^2 + 4)}{(s^2 + 9)} \xrightarrow{\text{confrac}} \begin{bmatrix} 0 & s \\ \frac{9}{4} & s^2 \\ \frac{16}{31} & s^2 \\ \frac{961}{60} & 0 \end{bmatrix} \xrightarrow{\text{parfrac}} s + \frac{15 \cdot s}{4 \cdot (s^2 + 4)} + \frac{9}{4 \cdot s}$$

$$\left( s + \frac{15 \cdot s}{4 \cdot (s^2 + 4)} \right)^{-1} \xrightarrow{\text{parfrac}} \frac{16}{31 \cdot s} + \frac{60 \cdot s}{31 \cdot (4 \cdot s^2 + 31)}$$


$$\left( \frac{60 \cdot s}{31 \cdot (4 \cdot s^2 + 31)} \right)^{-1} \xrightarrow{\text{parfrac}} \frac{31 \cdot s}{3 \cdot 5} + \frac{961}{60 \cdot s}$$

C2

$$Z(s) := \frac{(s^2 + 1)}{s} \cdot \frac{(s^2 + 9)}{(s^2 + 4)} \xrightarrow{\text{parfrac}} s + \frac{15 \cdot s}{4 \cdot (s^2 + 4)} + \frac{9}{4 \cdot s}$$

$$\frac{1}{\frac{15 \cdot s}{4 \cdot (s^2 + 4)} + \frac{9}{4 \cdot s}} \xrightarrow{\text{parfrac}} \frac{s}{2 \cdot 3} + \frac{5 \cdot s}{6 \cdot (2 \cdot s^2 + 3)}$$

$$\textcircled{\phantom{L}} L_1 := 1$$

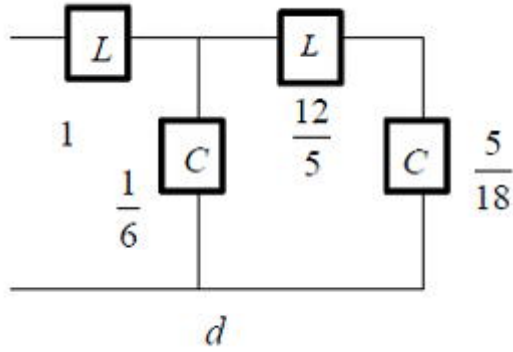

$$\textcircled{\phantom{C}} C_1 := \frac{1}{6}$$

$$\frac{1}{5 \cdot s} \xrightarrow{\text{parfrac}} \frac{12 \cdot s}{5} + \frac{18}{5 \cdot s}$$

$$\frac{1}{6 \cdot (2 \cdot s^2 + 3)}$$

$$s \cdot L_1 + \frac{1}{s \cdot C_1 + \frac{1}{s \cdot L_2 + \frac{1}{s \cdot C_2}}}$$

$$\textcircled{\phantom{L}} L_2 := \frac{12}{5} \quad \textcircled{\phantom{C}} C_2 := \frac{5}{18}$$

$$Z(s) := \frac{(s^2 + 1)}{s} \cdot \frac{(s^2 + 9)}{(s^2 + 4)} \xrightarrow{\text{parfrac}} s + \frac{15 \cdot s}{4 \cdot (s^2 + 4)} + \frac{9}{4 \cdot s}$$

$$\left( \frac{15 \cdot s}{4 \cdot (s^2 + 4)} + \frac{9}{4 \cdot s} \right)^{-1} \xrightarrow{\text{parfrac}} \frac{s}{2 \cdot 3} + \frac{5 \cdot s}{6 \cdot (2 \cdot s^2 + 3)}$$

$$\left( \frac{5 \cdot s}{6 \cdot (2 \cdot s^2 + 3)} \right)^{-1} \xrightarrow{\text{parfrac}} \frac{12 \cdot s}{5} + \frac{18}{5 \cdot s}$$