
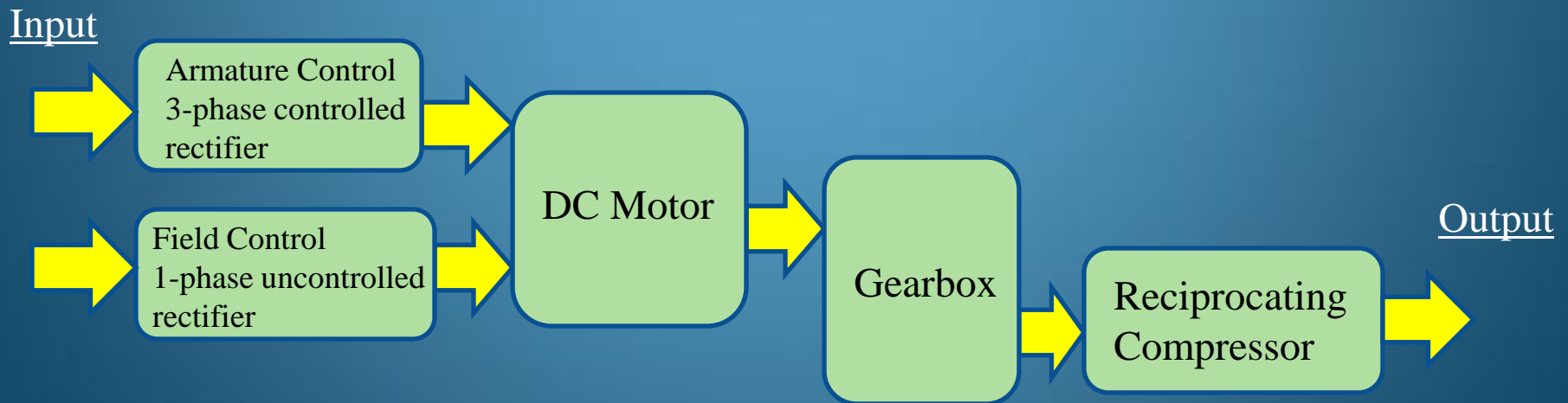


Mathcad – Assignment System Calculation

Dr Malcolm W. Renton

Compressor Drive System

- Block Diagrams:

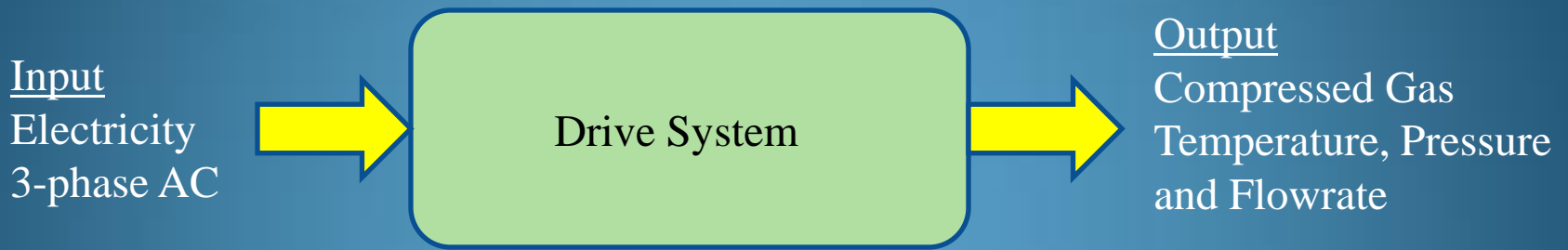


AC-DC Rectifier


- Converts Alternating Current to Direct Current
- Two basic types:
 - Half-Wave
 - Full-Wave
- Two modes of operation:
 - Uncontrolled
 - Controlled
- Used throughout industry, commerce and domestic installations

Half Wave and Full Wave

- Half-Wave:

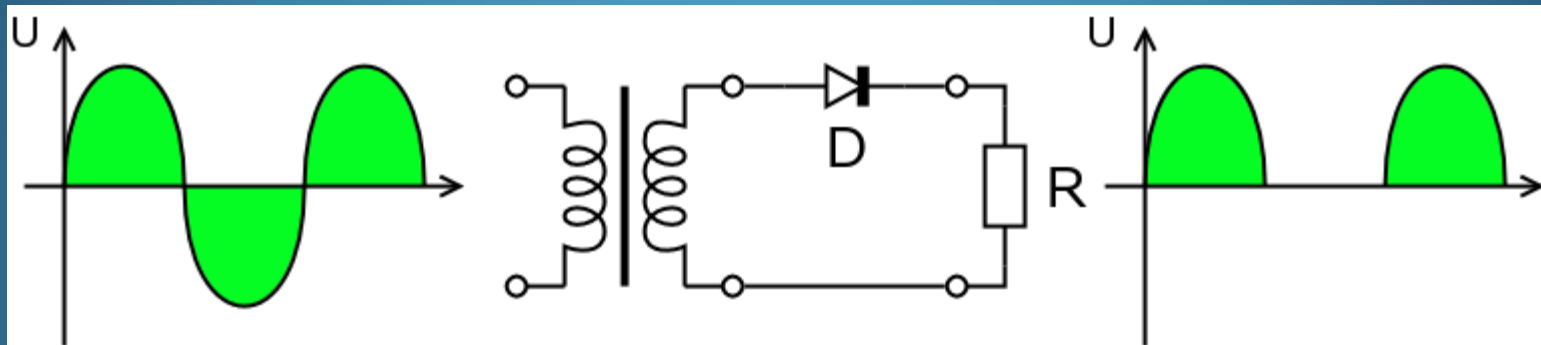


- Full-Wave:

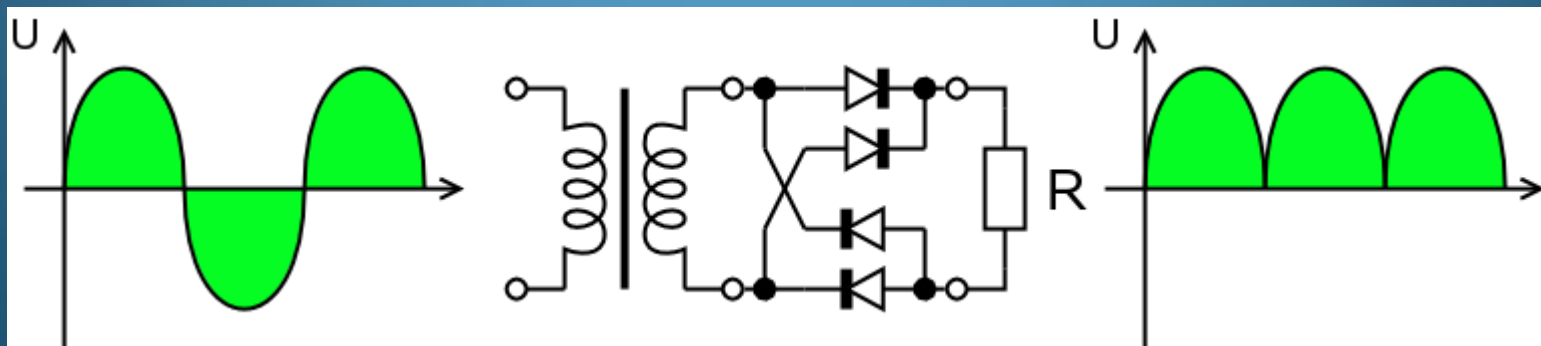



Uncontrolled Rectifier

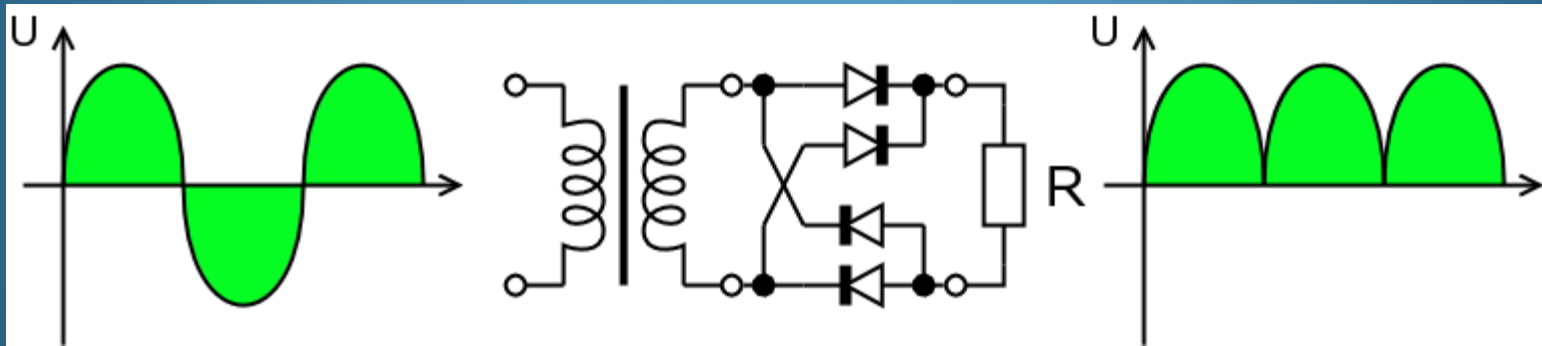- Diodes conduct when cathode (K) voltage is greater than the anode (A).



- Governing Equation:
- Single-Phase supply $E_{DC} = 0.9E_{AC}$


Three-Phase Uncontrolled rectifier

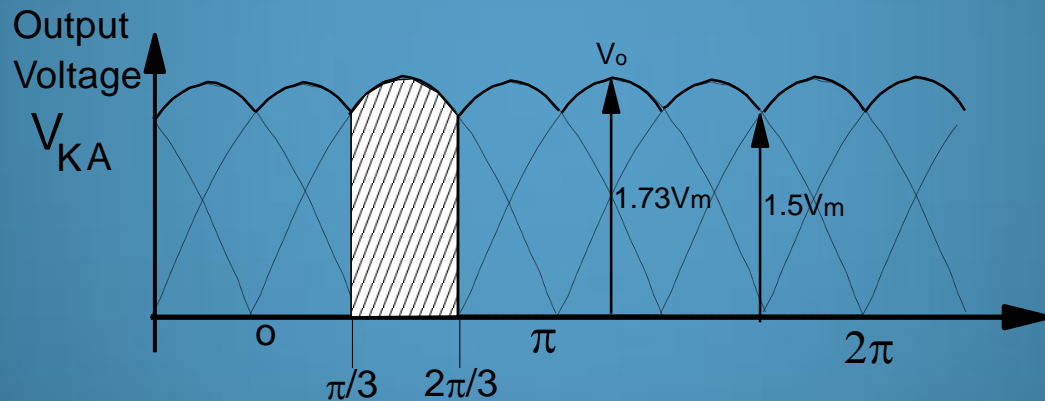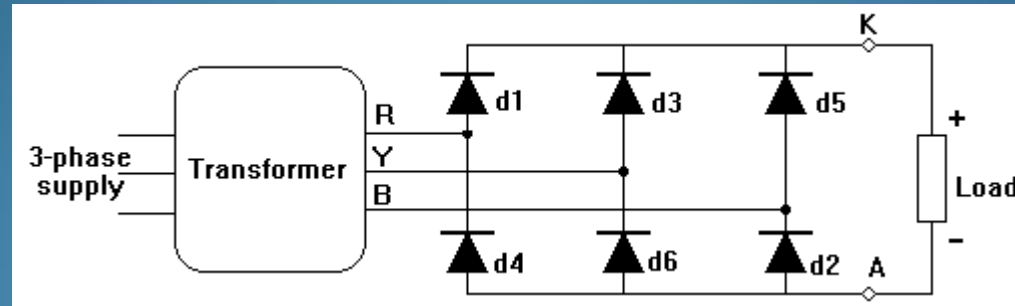

- Governing Equation:
- Three-Phase Supply: $V_{KA} = 1.35E_{AC}$
- or $E_{DC} = 1.35E_{AC}$


Controlled Rectifier

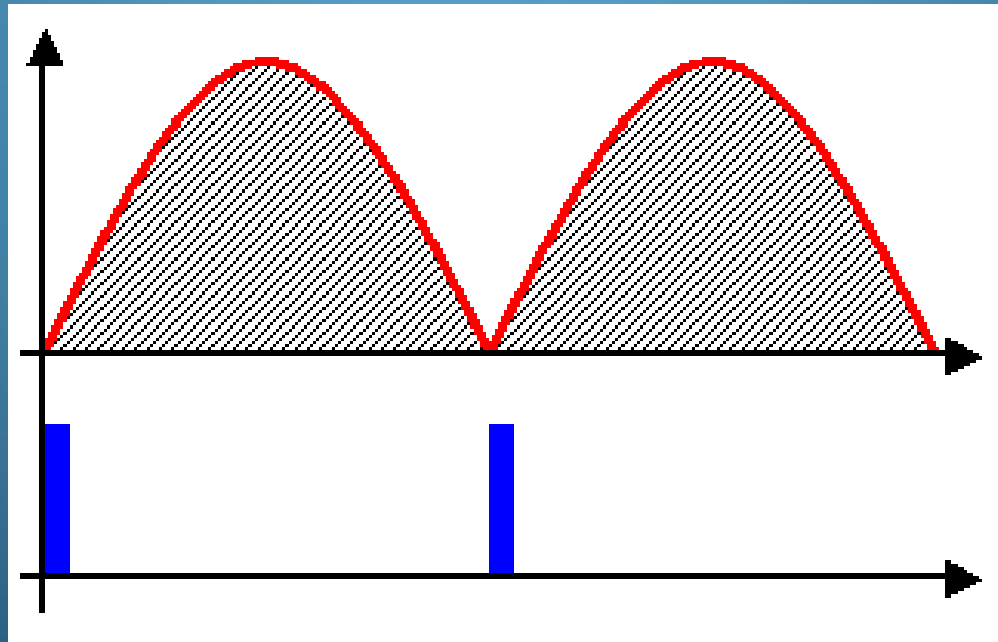- Transistors or Thyristors instead of Diodes
- Timed switching, controls output D.C. Level
- Single-phase supply $E_{DC} = 0.87E_{\max AC} \cos(\alpha)$
 - where α is the firing angle of the thyristor




3-phase Controlled Rectifier

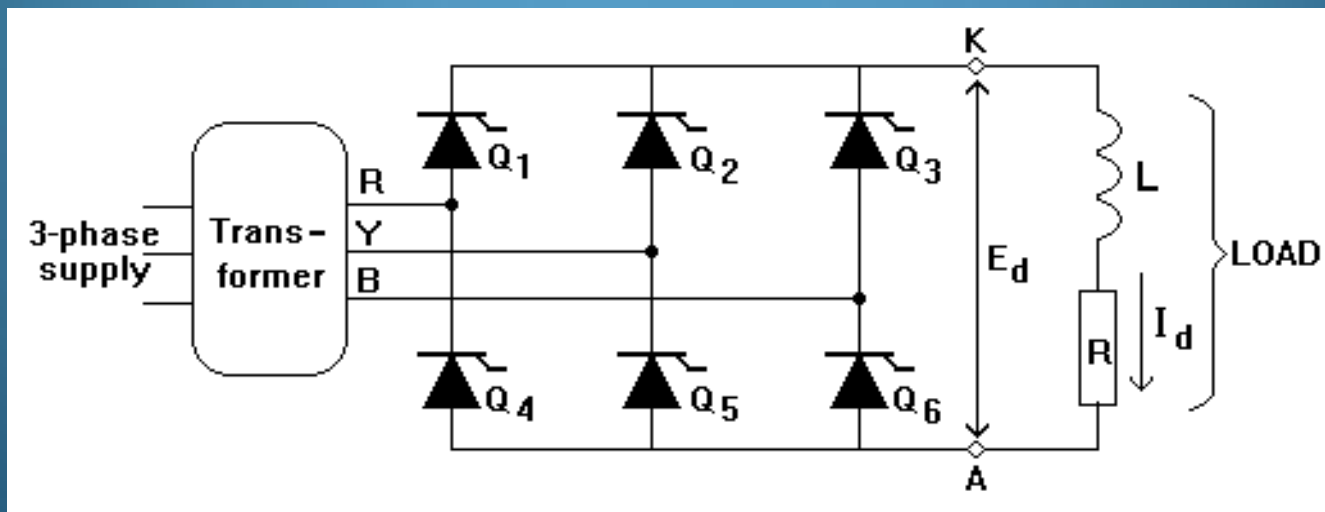- Three or Six Thyristors instead of Diodes
- Governing Equation
- $E_{DC} = 1.35 E_{AC} \cos(\alpha)$




Firing Angle Control


- Increasing firing angle: 0°

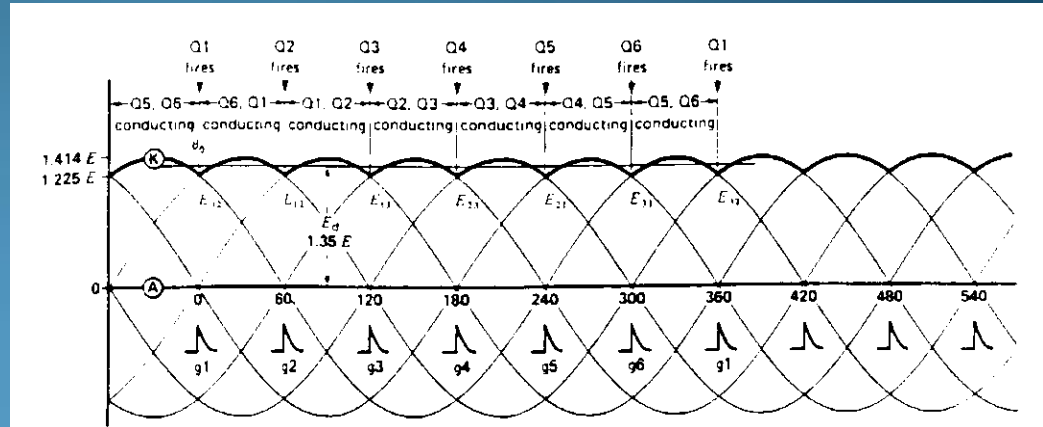

15°

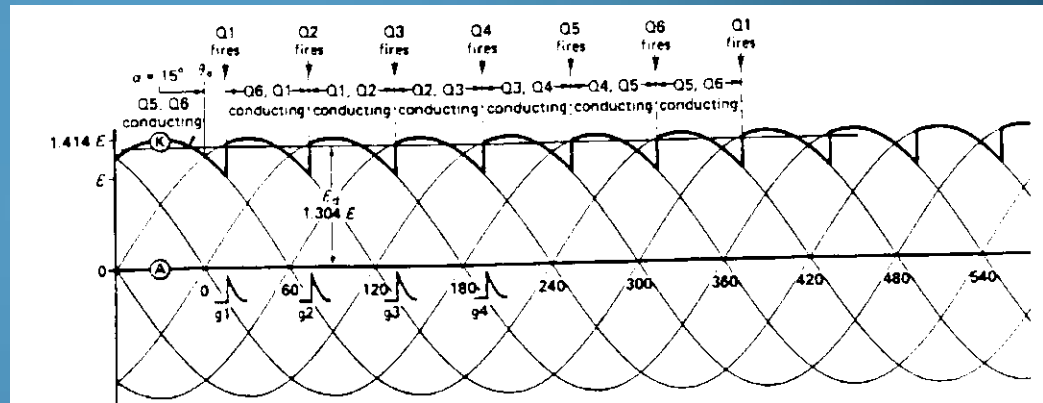

45°

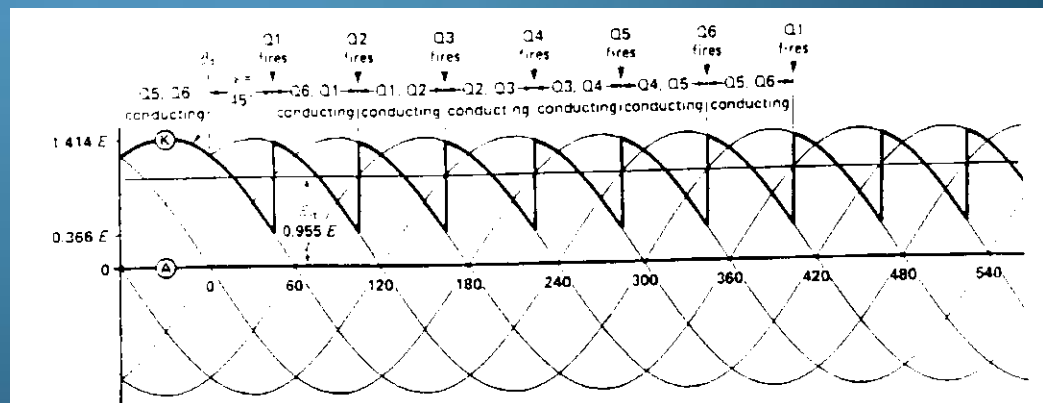

Rectifier Arrangements

- Simple Uncontrolled Bridge >



- Power Rectifier >



DC Motors




DC Machine (Motor)


- Comprises two windings (coils) through which current flows:
 - Armature (has resistance R_a and current I_a)
 - Field (has resistance R_f and current I_f)
- Different characteristics of motor due to the connection arrangement of the two windings:
 - Shunt
 - Series
 - Separate
 - Compound (cumulative or differential)

Separately Excited

- Schematic Diagram:

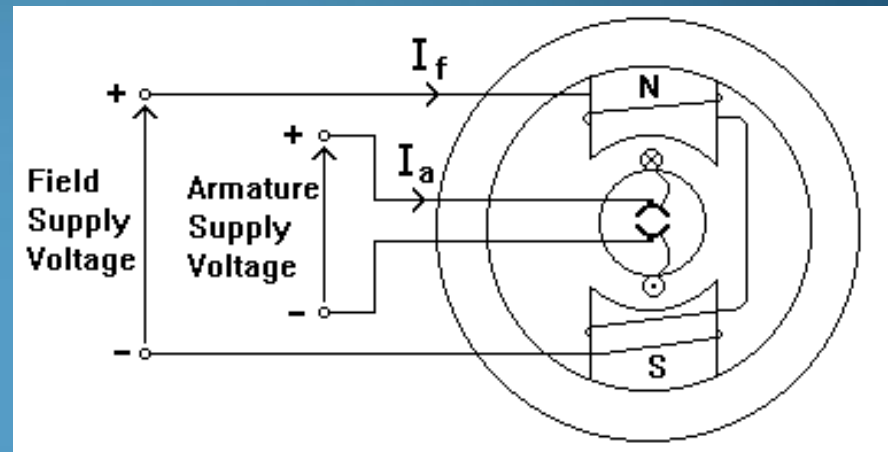

- Equivalent circuit:

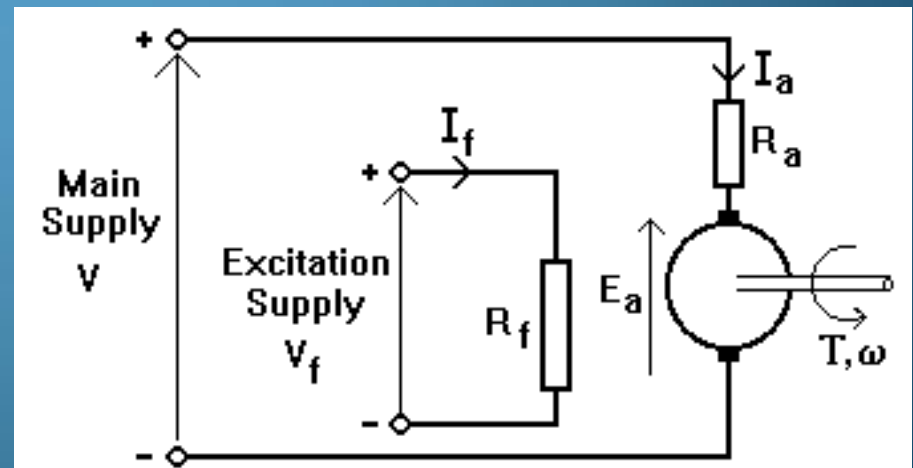

Governing Equations

- Basic Eqⁿ : $E_a = V - I_a.R_a$ and $V_f = I_f.R_f$
- Proportionality :
 - $T \propto \phi.I_a$ and $E_a \propto \phi.N$
- Also flux $\phi \propto I_f$ thus
 - $T \propto I_f.I_a$ and $E_o \propto I_f.N$
- Vary voltage (field or armature) to vary speed
- Reverse voltage – reverse speed

DC Motor Constants

- Constant k associated with the machine internal arrangement:
 - Number of coils (z)
 - Number of pole pairs (p) – (no. of poles/2)
 - Coil arrangement (c)
 - $2p$ for lap wound
 - 2 for wave wound
- $k = (z \cdot 2 \cdot p) / (60c)$
- Hence: $T = k \cdot \phi \cdot I_a$ and $E_a = k \cdot \phi \cdot N$
- Also flux $\phi = k_{\text{mag}} I_f$ where k_{mag} is the flux/amp.

DC Motor Power

- A motor converts electrical energy to mechanical energy
- Equating the previous proportional relationships:
- Electrical $E_a \cdot I_a = T \cdot \omega$ Mechanical
- Note: This is the developed power of the motor
- The output power is less,
 - due to mechanical efficiency
 - i.e. Friction and windage losses

Gearboxes

- Devices to change speed, direction and or alignment.





Gearbox Equation

- The gear ratio (e.g. 3:1) is the ratio of input/output speed
 - also the inverse ratio of gear teeth on the gearwheels
 - and the inverse ratio of input/output torque
- In an ideal gearbox $\text{Power in} = \text{Power out}$
- When efficiency is less than 100%, power out and output torque are reduced
 - but speed remains the same!

Crank Shaft

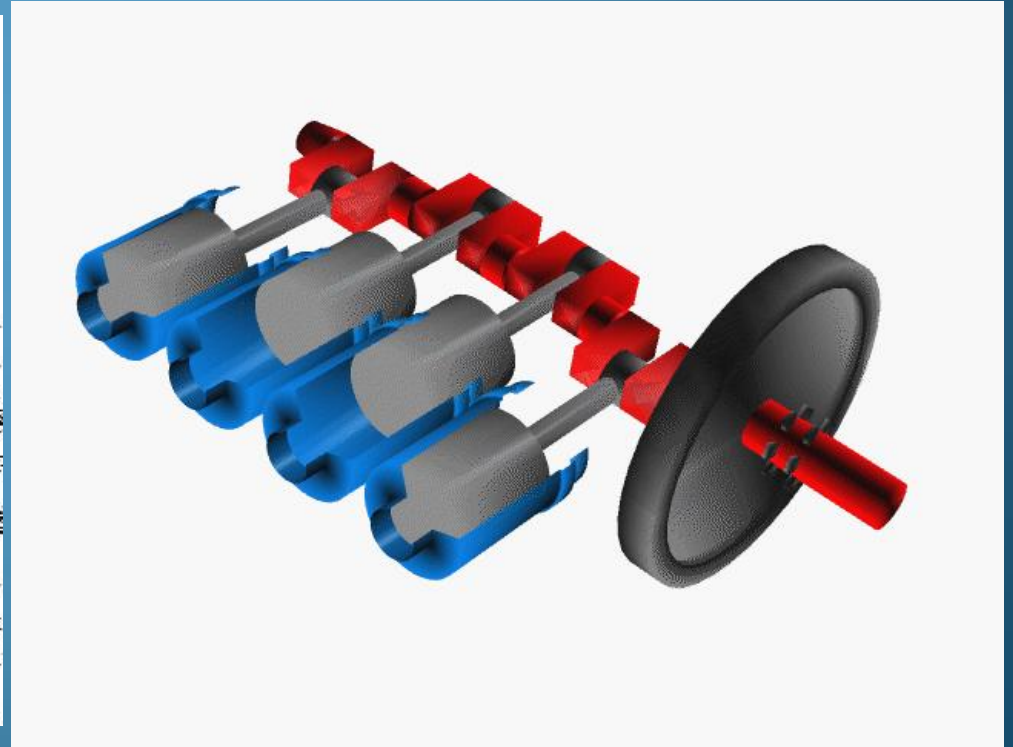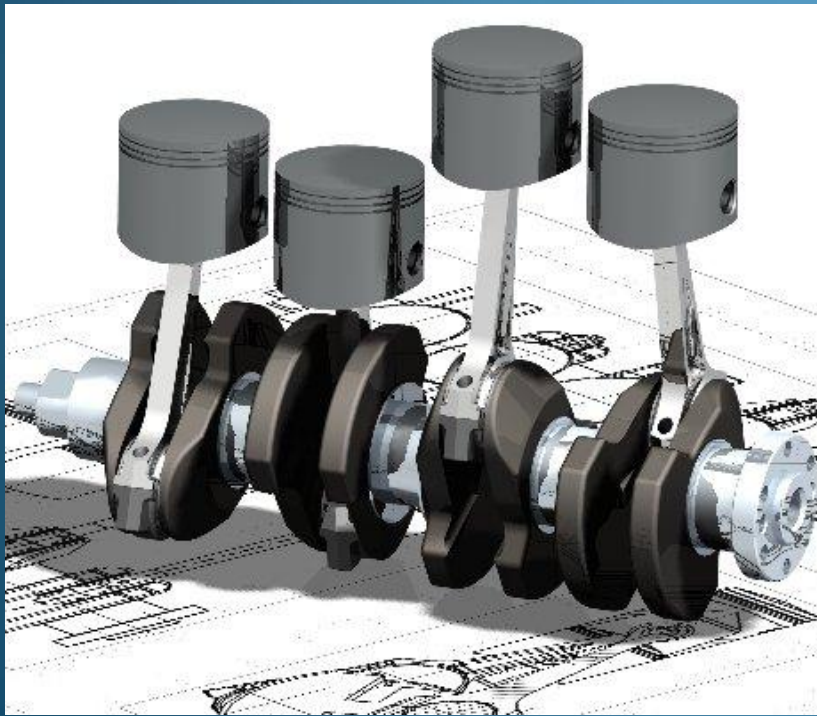- Physical connection between a rotating shaft and a reciprocating piston





Camshaft Geometry

l = rod length
 r = crank radius (half stroke)
 A = crank angle (from TDC)
 x = position of piston pin from crank center

$$l^2 = r^2 + x^2 - 2.r.x.\cos(A)$$

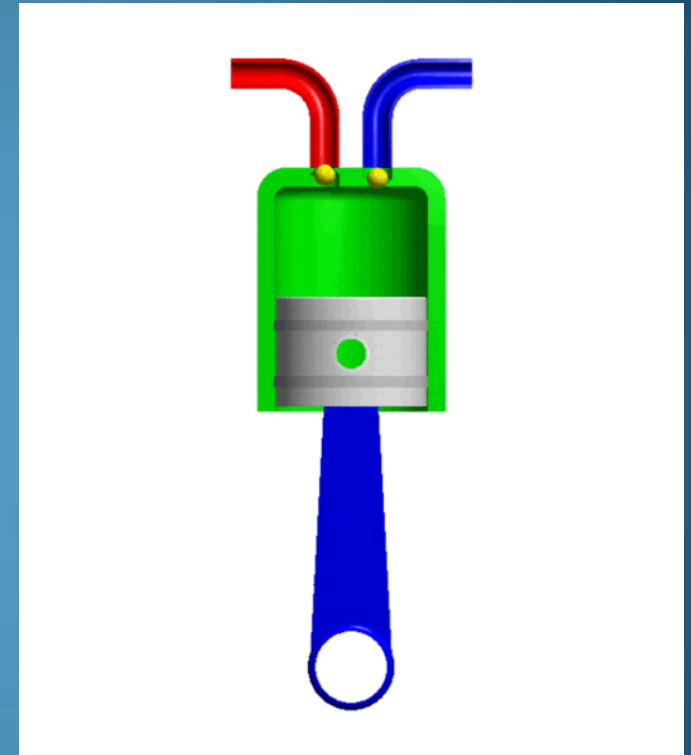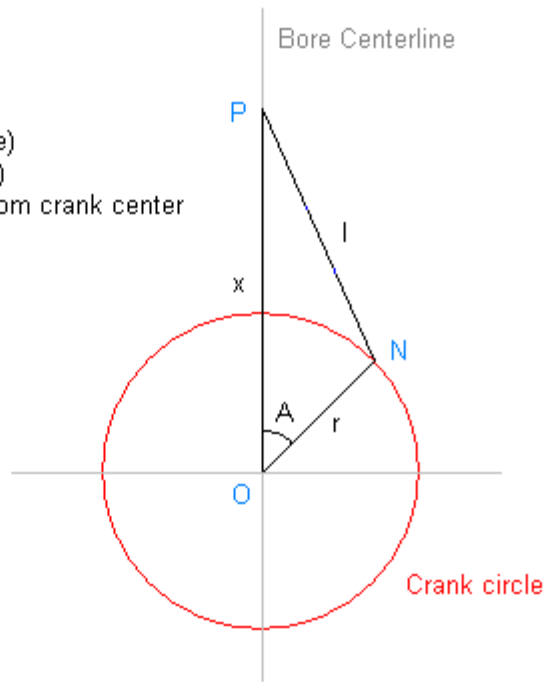
P : piston pin
N : crank pin
O : crank center



- Relationships associated with displacement, velocity and acceleration can be developed from this diagram

Reciprocating Compressor

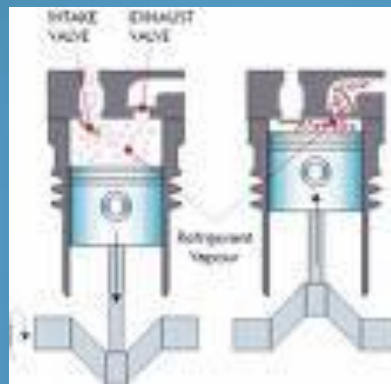- Device that uses pistons to compress fluid



- Operation depends on camshaft speed, physical dimensions of the pistons, fluid intake conditions and Gas Laws

Properties

- Pressure (p) in bar or Pa
- Temperature (T) in degrees Kelvin (K)
- Gas Constant R in (Nm/kgK)
- Polytropic index (n) – characteristic of fluid
- Mass flow rate (m) in kg/min
- Volume flow rate (V) in m^3/min
- Stroke (l) - length of piston in metres
- Bore (d) – diameter of piston in metres

Governing Equations

$$\text{Piston Volume} = \frac{\pi}{4} d^2 l$$


$$PV = \dot{m}RT$$

$$\frac{T_2}{T_1} = \left(\frac{p_2}{p_1} \right)^{\frac{(n-1)}{n}}$$


$$\text{indicated work} = \frac{n}{n-1} \dot{m}R(T_2 - T_1) \quad \text{kJ/min}$$

Reciprocating Compressor

- V arrangement

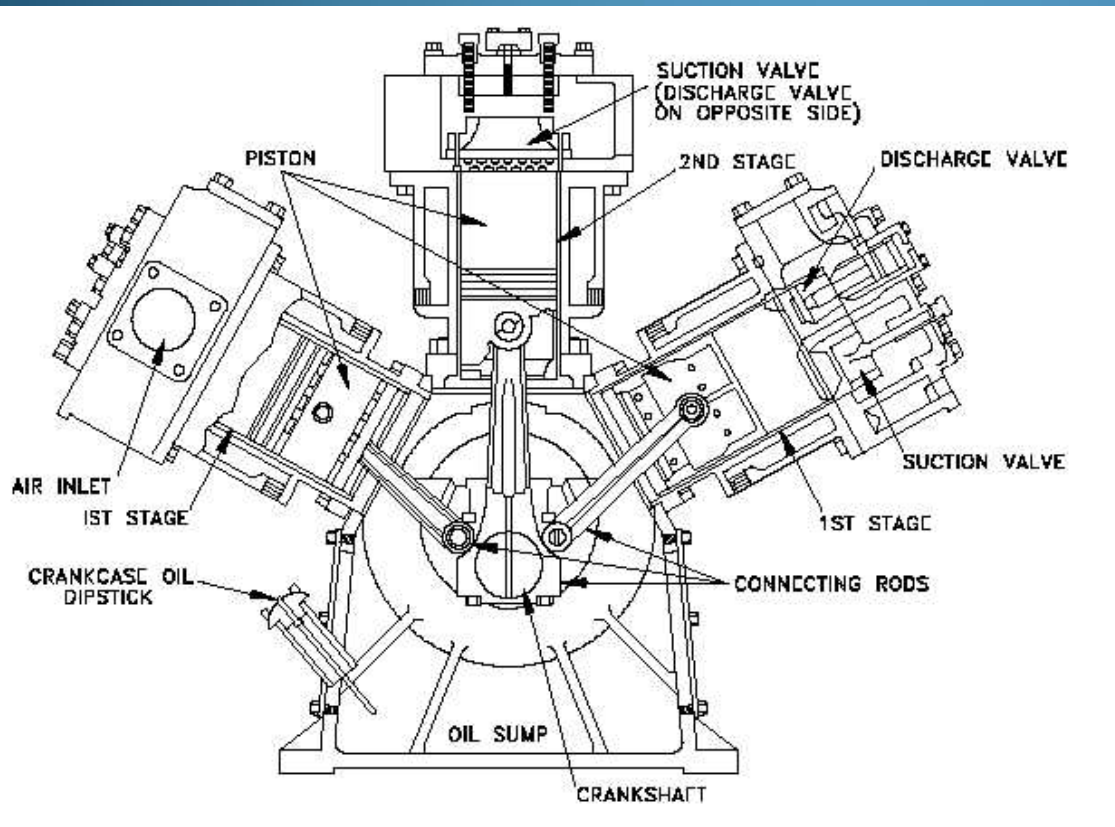

Complete System

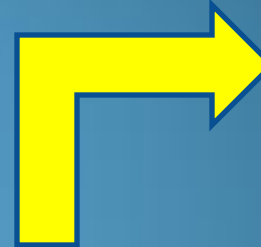

Assignment

- For rectifier firing angles from 0° to 60° determine:
 - Motor speed and output torque
 - Compressor mass flow rate
 - Compressor output temperature and pressure
- Use plot(s) to show the variation of these with firing angle of the rectifier.

Equipment Details

- AC Supply
 - 415V, 3-phase, 50 Hz

$$\text{Note } V_{1\text{-phase}} = \frac{V_{3\text{-phase}}}{\sqrt{3}}$$

- Motor
 - 6-pole, lap-wound separately-excited
 - $R_a = 0.2 \Omega$, $R_f = 200 \Omega$
 - Mechanical efficiency = 95%
 - $k_{\text{mag}} = 0.2 \text{ Wb/A}$
 - $I_a = 80 \text{ A}$ at full volts (0° firing angle)
 - assume I_a varies in proportion with E
 - Number of conductors = 720

Equipment Details

- Gearbox
 - Gear ratio 3:1
 - Efficiency = 92%
- Compressor
 - Efficiency = 90%
 - 2 cylinder each with a bore of 200 mm
 - Stroke/bore ratio = 1.9:1
 - Intake at atmospheric conditions 1.013 bar, 15°C
 - $R = 287$ (Nm/kgK) and $n = 1.35$