

# UCC3817/8A Design Procedure

Michael O'Loughlin  
Applications Engineer  
UCC3817 MathCAD Design Tool  
7-29-08

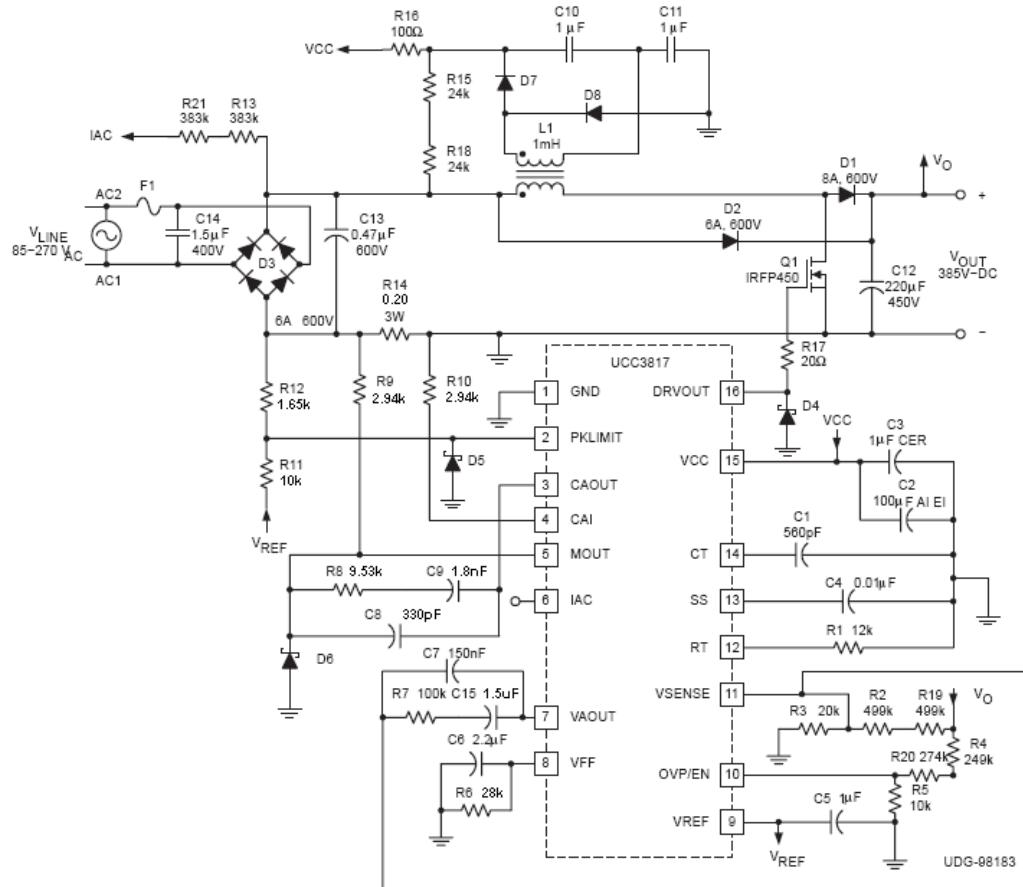


Figure 1. Typical Application Circuit

## I. Power Factor Pre regulator Design:

### 1. PFC Design Goals:

$V_{inmin} := 85V$        $V_{in}$  Minimum

$V_{inmax} := 265V$        $V_{in}$  Maximum

$V_{out} := 385V$       Output Voltage

$P_{out} := 250W$       Output Power

$\eta_1 := 0.95$       Note  $\eta$  represents efficiency  
a.)  $\eta_1$  is the estimated PFC efficiency

$f_s := 100 \cdot 10^3 Hz$

$V_{ovp} := 425V$       Over Voltage Protection Trip Point

2. Device Parameters:

$$V_{rmsmin} := 1.4V \quad V_{rmsmax} := 5V \quad V_{ref} := 7.5V \quad V_{eamin} := .5V \quad V_{eamax} := 5.5V \quad V_p := 4V$$

3. Select a Boost Inductor L1( $L_{BOOST}$ ):

a. Calculate Peak Input Current

$$I_{pk} := \sqrt{2} \cdot \frac{\frac{P_{out}}{\eta_1}}{V_{inmin}}$$

$$I_{pk} = 4.378 A$$

$$dI := .20 \cdot I_{pk}$$

$$dI = 0.876 A$$

b. Calculate Maximum Duty Cycle

$$D := \frac{V_{out} - \sqrt{2} \cdot V_{inmin}}{V_{out}}$$

$$D = 0.688$$

c. Calculate Inductance

$$L_1 := \frac{V_{inmin} \cdot \sqrt{2} \cdot D}{dI \cdot f_s}$$

$$L_1 = 9.441 \times 10^{-4} H$$

d. Select an Inductance Close to the Calculated Value

$$L_1 := 1.0 \cdot 10^{-3} H$$

4. Select a High Voltage Capacitor C12 ( $C_{OUT}$ ):

a. Choose a Minimum Hold up Time for 60Hz

$$t_{holdup} := 16 \cdot 10^{-3} s$$

b. Select Amount of Voltage Droop that is Allowed During Hold up Time

$$V_{pfc\_Droop} := 85V$$

c. Calculate PFC DC Current

$$I_{dc} := \frac{P_{out}}{V_{out}}$$

$$I_{dc} = 0.649 A$$

d. Calculate Minimum Capacitance Needed

$$C12 := \frac{2 \cdot \frac{P_{out}}{\eta_1} \cdot t_{holdup}}{V_{out}^2 - (V_{out} - V_{pf\_Droop})^2}$$

$$C12 = 1.446 \times 10^{-4} \cdot F$$

d. Choose a Capacitor > or = the Minimum Capacitance For Your Design

$$C12 := 220 \cdot 10^{-6} F$$

## 5. Select Timing Components ( $R_T$ and $C_T$ ) for 100 kHz switching frequency

Let  $C1 = 12$  kohm

$$R1 := 12 \cdot 10^3 \text{ ohm}$$

$$C1 := \frac{.6}{R1 \cdot f_s}$$

$$C1 = 5 \times 10^{-10} \cdot F$$

a. Choose a Capacitor Close to a Standard Value

$$C1 := 560 \cdot 10^{-12} F$$

## 6. Select Components for $V_{rms}$ Filter:

$$I_{acmax} := 500 \cdot 10^{-6} A$$

$$R_{iac} := V_{inmax} \cdot \frac{\sqrt{2}}{I_{acmax}}$$

$$R_{iac} = 7.495 \times 10^5 \cdot \text{ohm}$$

$$R_{iac} := 2 \cdot 383 \cdot 10^3 \text{ ohm} \quad \text{Select Two Resistors to Meet Voltage Requirements}$$

$$R_{iac} = R_{21} + R_{13}$$

**DC current through  $V_{rms}$  is 1/2 lac current (2:1 mirror) X 0.9 (dc factor) = 250uA X 0.9**

$$R_{VFF} := \frac{1.4V}{\frac{V_{inmin}}{R_{iac} \cdot 2} \cdot 0.9}$$

$$R_{VFF} = 2.804 \times 10^4 \cdot \text{ohm}$$

$$R_{VFF} = R_6$$

a. Choose an  $R_{VFF}$  ( $R_6$ ) Resistor Close to a Standard Value

$$R_{VFF} := 28.0 \cdot 10^3 \text{ ohm}$$

$$R_6 = R_{VFF}$$

b. Calculate the Needed  $C_{VFF}$  Capacitance

The allowable contribution to THD from  $V_{rms}$  is 1.5%. The second harmonic is 66% of the fundamental, so to reduce the contribution to 1.5% the  $V_{rms}$  filter must have a gain of 1.5% / 66% or .022. Back-calculating the frequency of a pole which will give the necessary attenuation at 120Hz places the pole at 2.6Hz.

$$f_p := 2.6 \text{Hz}$$

$$C_{VFF} := \frac{1}{2 \cdot \pi \cdot R_{VFF} \cdot f_p}$$

$$C_{VFF} = 2.186 \times 10^{-6} \cdot F$$

c. Choose an  $R_{VFF}$  ( $C_6$ ) Resistor Close to a Standard Value

$$C_{VFF} := 2.2 \cdot 10^{-6}$$

$$C_{VFF} = C_6$$

7. Size current sense resistor (R14) for a 1V dynamic range.

$$Rsense := \frac{1V}{Ipk + 0.5 \cdot dI}$$

$$Rsense = 0.208 \cdot \text{ohm}$$

Choose a standard value

$$Rsense := 0.20\text{ohm}$$

$$Rsense = R14$$

8. Multiplier Set up

$$Iac\_at\_Vinmin := Vinmin \cdot \frac{\sqrt{2}}{Riac}$$

$$Iac\_at\_Vinmin = 1.569 \times 10^{-4} \text{ A}$$

I<sub>mo</sub> at low line is determined by I<sub>ac\_lowline</sub>, V<sub>eamax</sub>, and V<sub>rmsmin</sub>.

$$Km := \frac{1}{V}$$

$$Imomax := \frac{Iac\_at\_Vinmin \cdot (Veamax - 1V)}{Km \cdot Vrmsmin^2}$$

$$Imomax = 3.603 \times 10^{-4} \cdot \text{A}$$

The power limit for the forward converter is set to roughly 120% of the output power. To reduce instabilities the power limit needs to be set greater than 120%.

$$Plimit := \frac{Pout \cdot (1.2)}{\eta 1}$$

$$Plimit = 315.789 \cdot \text{W}$$

$$Vrs := \frac{Plimit \cdot \sqrt{2}}{Vinmin} \cdot Rsense$$

$$Rmout := \frac{Vrs}{Imomax}$$

$$R_{mout} = 2.917 \times 10^3 \cdot \text{ohm}$$

a. Choose a standard value resistor resister close to the calculated value.

$$R_{mout} := 2.94 \cdot 10^3 \text{ ohm}$$

$$R_{mout} = R9, R10$$

#### 9. Select Components for Pulse by Pulse Current limiting:

a. Choose a Peak Power Limit.

Remember this limit has to be higher than the power limit that the multiplier provides.

$$I_{limit} := \frac{P_{out} \cdot (1.3) \cdot (\sqrt{2})}{V_{inmin} \cdot (\eta_1)} + 0.5 \cdot dI$$

$$V_{rs} := I_{limit} \cdot R_{sense}$$

b. Calculate Ipeak Resistor Divider

$$R_{11} := 10 \cdot 10^3 \text{ ohm}$$

$$R_{12} := \frac{V_{rs} \cdot R_{11}}{V_{ref}}$$

$$R_{12} = 1.635 \times 10^3 \text{ ohm}$$

Choose a standard resistor value

$$R_{12} := 1.65 \cdot 10^3 \text{ ohm}$$

#### 10. Current Loop Design

a. Gain of the PFC Power Stage is:

$$G_{id}(s) = \frac{V_{out} \cdot R_{sense}}{s \cdot L_{boost} \cdot V_p}$$

b. Solving for the power stage gain at the desired crossover frequency of 10 kHz in the frequency domain yields:

$$f_c := 10 \cdot 10^3 \text{ Hz}$$

$$G_{id} := \frac{V_{out} \cdot R_{sense}}{2 \cdot \pi \cdot f_c \cdot L_1 \cdot V_p}$$

$$G_{id} = 0.306$$

c. In order to have a gain of 1 at the crossover frequency the current amp must have a gain of  $1/G_{ps}$  at the crossover frequency.

$$G_{ea} := \frac{1}{G_{id}}$$

$$G_{ea} = 3.264$$

$$R_i := R_{mout}$$

$$R_f := R_i \cdot G_{ea}$$

$$R_f = 9.596 \times 10^3 \cdot \text{ohm}$$

$$C_z := \frac{1}{2 \cdot \pi \cdot f_c \cdot R_f}$$

$$C_z = 1.659 \times 10^{-9} \cdot \text{F}$$

$$C_p := \frac{1}{2 \cdot \pi \cdot R_f \cdot \left( \frac{f_s}{2} \right)}$$

$$C_p = 3.317 \times 10^{-10} \cdot \text{F}$$

c. Choose values for  $R_f$ ,  $C_z$ , and  $C_p$  closest to there calculated values

$$R_f := 9.53 \cdot 10^3 \text{ ohm} \quad C_z := 1.8 \cdot 10^{-9} \text{ F} \quad C_p := 330 \cdot 10^{-12} \text{ F}$$

$$R_f = R_8$$

$$C_z = C_9$$

$$C_p = C_8$$

## 11. Voltage Amplifier Loop Design:

a. We first determine how much ripple is on the output capacitor and then design the feedback to attenuate the ripple to .75% of THD.

$$v_{opk} := \frac{P_{out} \cdot \frac{1}{\eta_1}}{2 \cdot \pi \cdot 120\text{Hz} \cdot C_{12} \cdot V_{out}}$$

$$v_{opk} = 4.121 \cdot V$$

$$v_{opp} := v_{opk} \cdot 2$$

$$veapk := .015 \cdot (Veamax - Veamin)$$

$$veapk = 0.075 \cdot V$$

$$Gvea := \frac{veapk}{vopp}$$

$$Gvea = 9.1 \times 10^{-3}$$

b. Select Standard Components for the Voltage Loop Closest to their Calculated Values

$$Rin := 2 \cdot 499 \cdot 10^3 \text{ ohm} \text{ Let the input resistor equal } 1.12 \text{ Mohm.}$$

$$Rin = R22 + R23$$

$$Rd := \frac{Vref \cdot Rin}{Vout - Vref}$$

$$Rd = 1.983 \times 10^4 \cdot \text{ohm}$$

$$Rd := 20 \cdot 10^3 \text{ ohm}$$

$$Rd = R3$$

$$Cf := \frac{1}{2 \cdot \pi \cdot 120\text{Hz} \cdot Gvea \cdot Rin}$$

$$Cf = 1.46 \times 10^{-7} \cdot F$$

Choose a standard value for the feedback capacitor

$$Cf := 150 \cdot 10^{-9} F$$

$$Cf = C7$$

$$G_{ps\_fc} := \frac{P_{out}}{(V_{eamin} - V_{emax}) \cdot V_{out} \cdot 2 \cdot \pi \cdot C_{12}}$$

$$G_{ps\_fc} = 93.952 \cdot Hz$$

$$G_{vea1} := \frac{1}{2 \cdot \pi \cdot R_{in} \cdot C_p}$$

$$G_{vea1} = 483.254 \cdot Hz$$

$$T_v := G_{ps\_fc} \cdot G_{vea1}$$

$$T_v = 4.54 \times 10^4 \cdot Hz^2$$

$$f_{crossover} := \sqrt{T_v}$$

$$f_{crossover} = 213.079 \cdot Hz$$

$$R_f := \frac{1}{2 \cdot \pi \cdot f_{crossover} \cdot C_p}$$

$$R_f = 2.263 \times 10^6 \cdot ohm$$

Choose a standard resistor

$$R_f := 100 \cdot 10^3 ohm$$

$$R_f = R_7$$

$$C_z := \frac{1}{2 \cdot \pi \cdot \frac{f_{crossover}}{10} \cdot R_f}$$

$C_z$  removes proportional gain caused by Op Amp loading

$$C_z = 7.469 \times 10^{-8} \cdot F$$

$$C_z := 1.5 \cdot 10^{-6}$$

$$C_z = C_{15}$$

## 12. Setting up OVP/PFC Enable Divider

$$R_{bot} := 10 \cdot 10^3 \text{ ohm} \quad \text{Pick a resistor for } R_5$$

$$R_{bot} = R_5$$

$$R_5 := R_{bot}$$

$$V_{ovp} = 425 \cdot V$$

The high side of the OVP divider ( $R_{top}$ ) should be formed by two resistors

$$R_{top} := \frac{(V_{ovp} - 8V) \cdot R_{bot}}{8V}$$

$$R_{top} = 5.213 \times 10^5 \cdot \text{ohm}$$

Choose standard resistors that equal  $R_{top}$

$$R_{top} = R_{20} + R_4$$

$$R_{20} := 274 \cdot 10^3 \text{ ohm}$$

$$R_4 := 249 \cdot 10^3 \text{ ohm}$$

Check OVP

$$\frac{8V \cdot (R_5 + R_4 + R_{20})}{R_5} = 426.4 \cdot V$$

Check PFC Enable

$$\frac{1.9V \cdot (R_5 + R_4 + R_{20})}{R_5} = 101.27 \cdot V$$